



DEPARTMENT: Electrical & Computer Engineering DATE & TIME: 7th March 2011 at 1800
PAPER NO.: — PAGE NO.: 1 of 5
COURSE: ENG 1450—Intro. Elect. & Comp. Eng. EXAMINATION: Mid-term (20%)
DURATION: 1 Hour EXAMINERS: A. Gole / A. Major

INSTRUCTIONS:

- Do not remove the staple.
 - Closed-book exam. No books/notes allowed.
 - Calculators are NOT allowed.
 - Return both this booklet and the bubble sheet at the end of the examination.
 - This is a multiple choice examination and consists of 15 questions.
 - Mark your answer in pencil on the bubble sheet provided.
 - No marks will be given for working on this booklet.
 - Each correct answer has one mark and each wrong answer has zero marks.
 - No negative marks for wrong answer.
-

STUDENT NUMBER

PRINT YOUR NAME IN FULL ON THIS LINE

SIGNATURE

A01 (Prof. Gole) A02 (Prof. Major)

CIRCLE YOUR SECTION

E2-105 E2-110 E3-270

CIRCLE YOUR EXAMINATION ROOM

(n/a)

SEAT NUMBER

Mark	
Out of	15


DEPARTMENT: Electrical & Computer Engineering DATE & TIME: 7th March 2011 at 1800
 PAPER NO.: — PAGE NO.: 2 of 5
 COURSE: ENG 1450—Intro. Elect. & Comp. Eng. EXAMINATION: Mid-term (20%)
 DURATION: 1 Hour EXAMINERS: A. Gole / A. Major

1 What is V_{AB} if we have to spend 10 J of energy in order to move a charge of 1 mC from point B to point A?

- A) 10 V
- B) 600 V
- C) 10,000 V
- D) 36,000 V
- E) 120,000 V


2 In the circuit shown below the current i_x is?

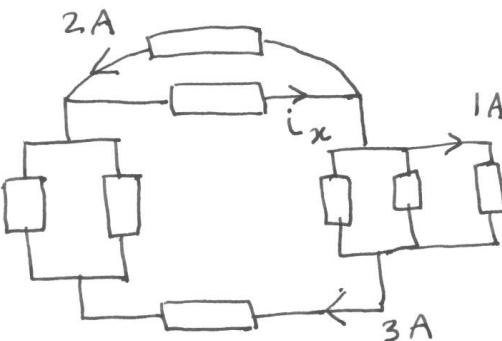- A) 4 A
- B) 1 A
- C) -1 A
- D) -6 A
- E) 5 A




3 What is $v_z + v_w$ in the circuit shown below?

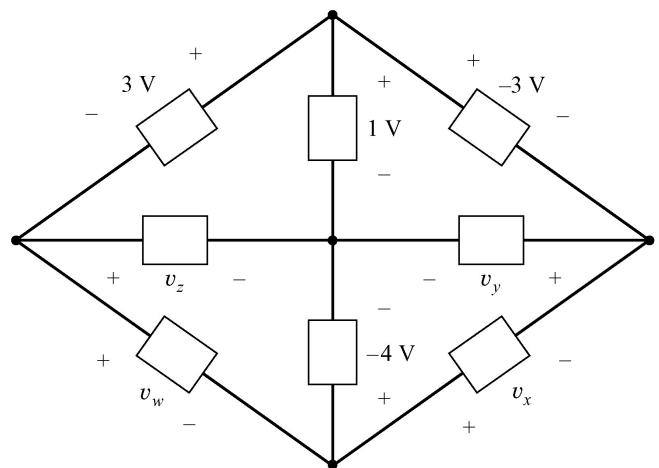- A) 0 V
- B) 4 V
- C) 2 V
- D) -2 V
- E) None of the above.



4 The power P absorbed by the 2Ω resistor is 8W. The current i can be assumed to be positive. The voltage v_2 is?

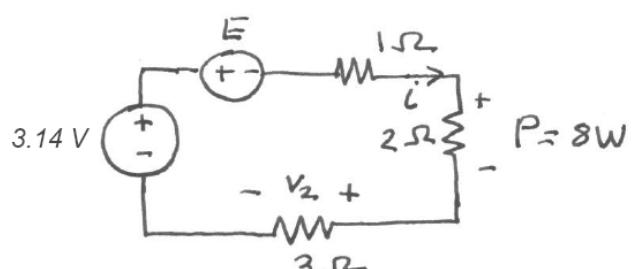- A) 3 V
- B) 6 V
- C) $3\sqrt{8}$ V
- D) 12 V
- E) -12 V



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 7th March 2011 at 1800

PAPER NO.: —

PAGE NO.: 3 of 5

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: A. Gole / A. Major

5 How much is the total power absorbed in the $4\ \Omega$ resistor?

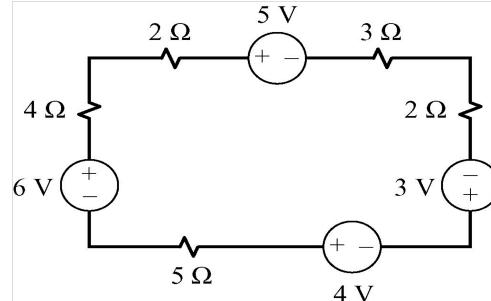- A) 0 W
- B) 2 W
- C) 36 W
- D) 1 W
- E) 8.32 W




6 We have two unknown resistors R_1 and R_2 . It is known that $R_2 = R_1/2$. It is also known that when we connect them in parallel the equivalent resistance is $2\ \Omega$. Find the resistance of R_2 . (Read question carefully...we are asking for R_2 only!)

- A) $6\ \Omega$
- B) $1\ \Omega$
- C) $3\ \Omega$
- D) $20\ \Omega$
- E) None of the above.


7 What is the equivalent resistance at terminals ab ?

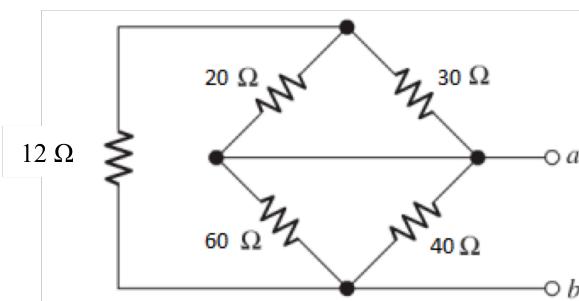- A) $12\ \Omega$
- B) $11.4\ \Omega$
- C) $15\ \Omega$
- D) $10\ \Omega$
- E) $28\ \Omega$




8 What is v_x in the circuit shown below?

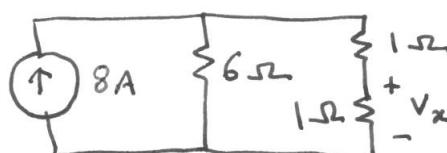- A) 4 V
- B) 2 V
- C) -4 V
- D) 6 V
- E) None of the above.



9 Determine the value of V_s if the $v_x = 5\text{ V}$.

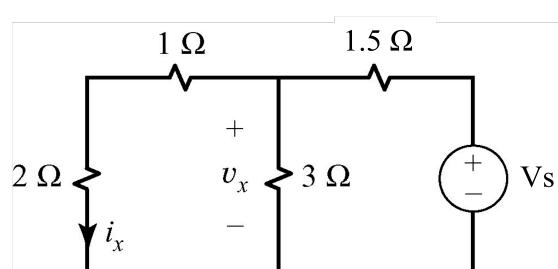
- A) 6 V
- B) 10 V
- C) 8 V
- D) 12 V
- E) None of the above.



DEPARTMENT: Electrical & Computer Engineering DATE & TIME: 7th March 2011 at 1800
 PAPER NO.: — PAGE NO.: 4 of 5
 COURSE: ENG 1450—Intro. Elect. & Comp. Eng. EXAMINATION: Mid-term (20%)
 DURATION: 1 Hour EXAMINERS: A. Gole / A. Major


10 How much power is absorbed/delivered by the (-1) A current source?

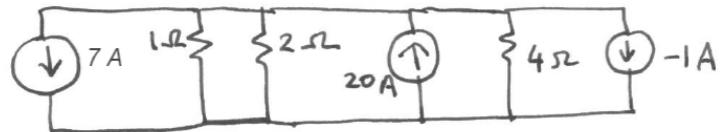- A) 7 W, delivered.
- B) 8 W, delivered.
- C) 3 W, delivered.
- D) 15 W, absorbed.
- E) 8 W, absorbed.




11 How much power is absorbed by a single 1-Ω resistor?

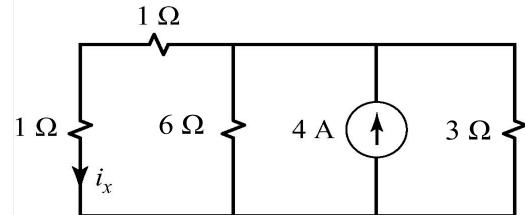- A) 1 W
- B) 33 W
- C) 16 W
- D) 10 W
- E) 4 W




12 What is the current i_x in the circuit given below?

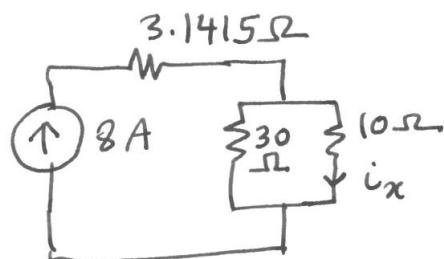- A) 6 A
- B) -3 A
- C) -1.214 A
- D) 14 A
- E) None of the above.



13 What is V_{AB} in the circuit shown below?

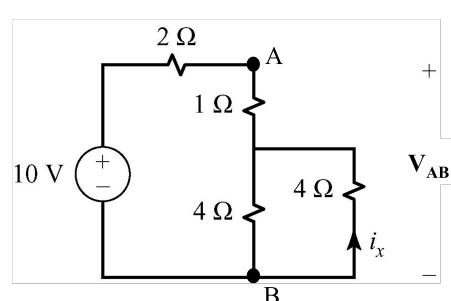- A) 10 V
- B) -4 V
- C) 1 V
- D) 6 V
- E) -3 V



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 7th March 2011 at 1800

PAPER NO.: —

PAGE NO.: 5 of 5

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: A. Gole / A. Major


- 14** In the opamp circuit shown, $R_i = 1 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$, and $V_s = 25 \text{ V}$. The output voltage V_{out} is:

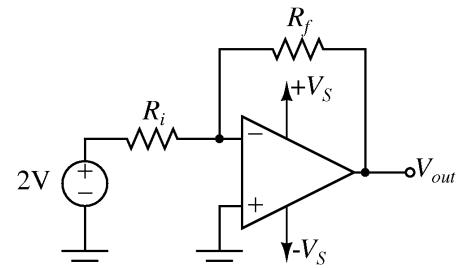- A) -20 V
- B) 20 V
- C) 2 V
- D) 0.2 V
- E) -0.2 V



- 15** A cross section of solenoid (a wire coil wrapped in a cylinder shape) is shown below. X and Y represent the upper and lower coil sections respectively. The magnetic field lines are as shown in the figure. What is the direction of a current flowing through the coil sections X and Y? (Directions: towards you, i.e. out of the page and the opposite one).

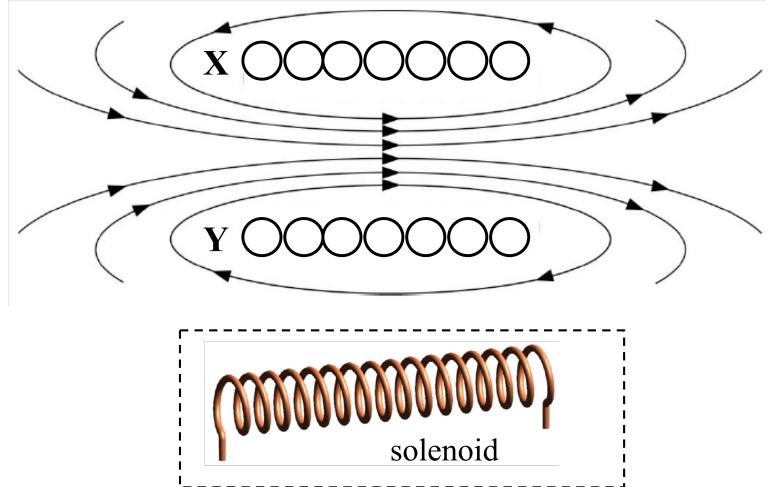- A) X: towards you, Y: towards you.
- B) X: away from you, Y: towards you.
- C) X: away from you, Y: away from you.
- D) X: towards you, Y: away from you.
- E) None of the above.



Formula Sheet

Ohm's law

$$V = RI$$

Power

$$P = VI$$

Energy

$$W = VQ$$

Voltage division

$$V_k = \frac{R_k}{\sum R_i} V_s$$

Current division

$$I_k = \frac{\frac{1}{R_k}}{\sum \frac{1}{R_i}} I_s$$

Resistors in series

$$R_{eq} = \sum R_i$$

Resistors in parallel

$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$

Energy stored in a capacitor

$$W = \frac{1}{2} CV^2$$